 


# Introduction to Bipolar Junction Transistors BJTs & DC Biasing Circuits

(Chapter 3&4 , Boylestad & Nashelsky)


- Transistors types
- Principles of Operation
- Main configurations
- Current Voltage Characteristics
- Limits of operation
- Biasing and stability circuits
- Analysis of DC transistor circuits
- Transistor switching



BJT Common Emitter fixed bias configuration




# Semiconductor Transistor Types

## Chapter 3

 



## Bipolar Junction Transistors (BJT)

- npn transistor
- pnp transistor

   

  
## Field Effect Transistors (FET)

- Junction FET
- Metal Oxide Semiconductor (MOS) Transistors
- Complementary MOS (CMOS)







JFET

 

MOSFET

  
 
 
# Bipolar Junction Transistor (BJT)

Conduction is *by electrons*(negative charged)  
*and holes*(positive charge)




Cross section in a typical npn transistor, each region is different

   Emitter heavily doped, Base lightly doped, Collector large area




more  $-ve$  charge

 

P type, Majority are Holes

Minority are Electrons


free +

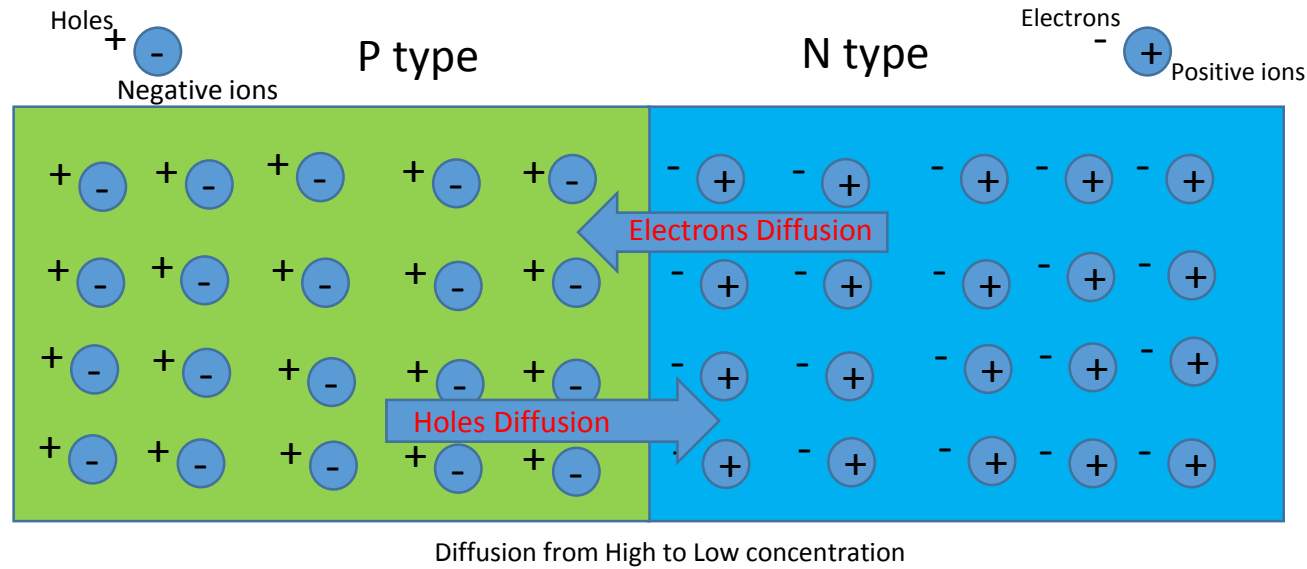

N type, Majority are Electrons


Minority are Holes

free -

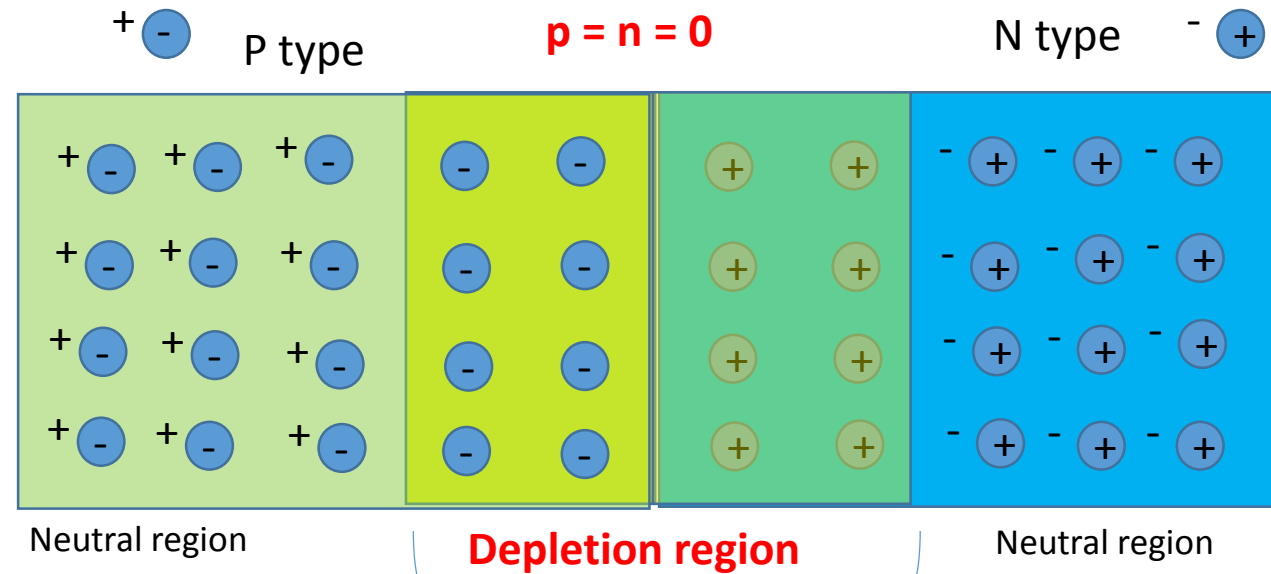


Depletion region, positive ions on N type side, negative ions on p type side. High electric field, built in potential, no free carriers, high resistance region

# pn junction under DC bias

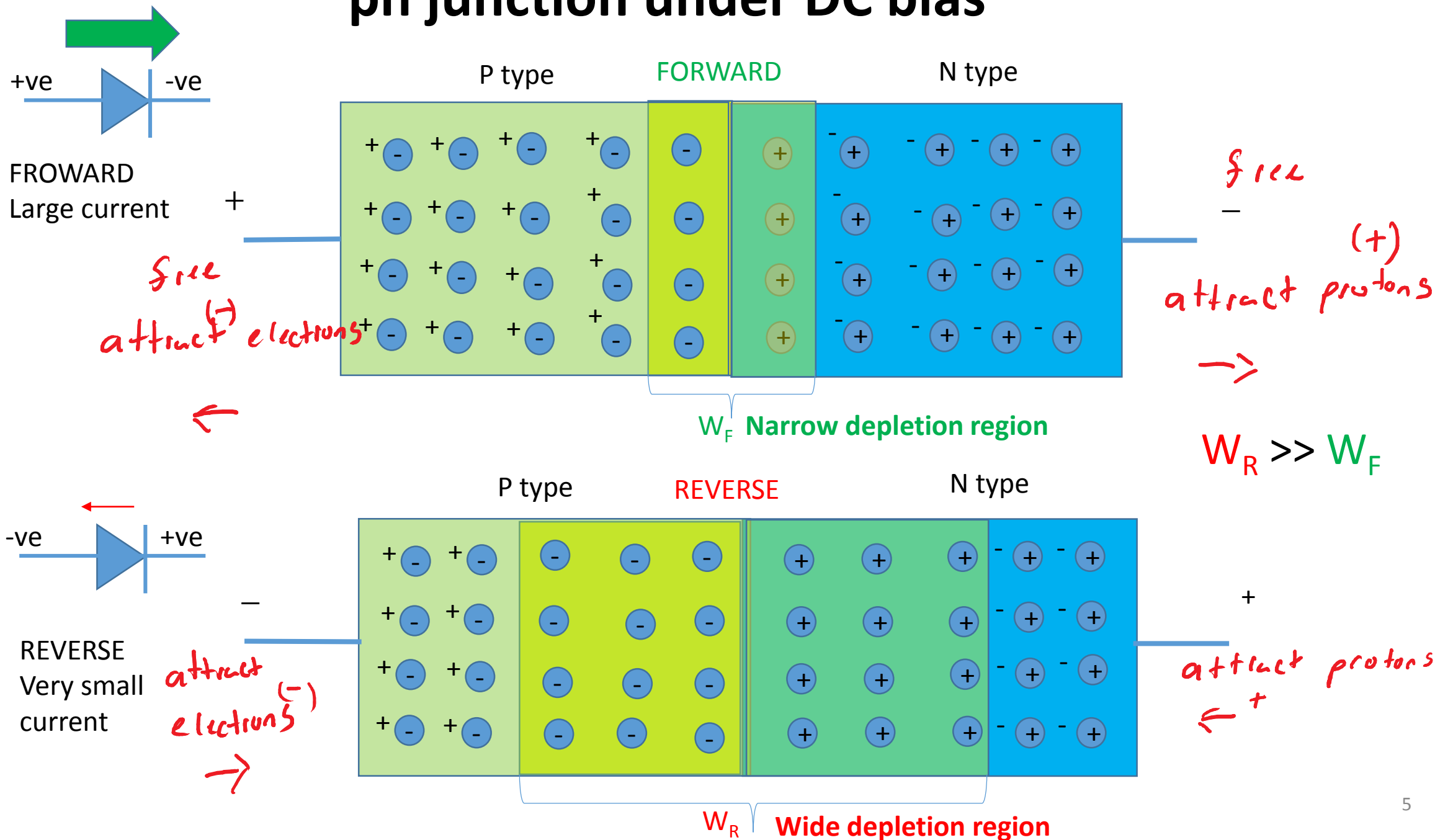

 
# Majority and Minority carriers flow of a pnp transistor.



$$I_E = I_C + I_B$$

Emitter current = Collector current + Base current

- E, Emitter
- B, Base
- C, Collector

 



- Holes(positive charge) in an p-type are the **Majority carriers** and electrons are the minority carriers.
- In an n-type, electrons(negative charge) are the **Majority carriers** and holes are the minority carriers.

# Transistor operations

Two junctions;

- Emitter-Base(EB) junction is forward biased (Majority carries flow)
- Collector-Base (CB) junction is reverse biased (Minority carries flow)
- BJTs are Current controlled devices(Base current  $I_B$  controls Collector current  $I_C$ )
- Emitter emits majority carriers(holes in p type) to the forward –biased EB junction, resulting in an emitter current  $I_E$  .
- The collector-base junction is reversed biased and only minority carriers flow(holes in n type).
- Emitted carriers (majority in p type) become minority in the base region ( n type)are collected at the collector terminal  $I_C$  .
- The base current  $I_B$  is the results of minority carriers , hence it is the smallest.
- Current flow direction is opposite to the electrons flow, i.e. current direction is same as holes( +ve charge) flow direction.
- Now applying Kirchhoff's Current Law, KCL :  $I_E = I_C + I_B$

  *“The sum of all currents flowing into a node equals the sum of currents flowing out of the node”.*








# Transistor Configurations

Three possible configurations:


- Common Emitter
- Common Collector
- Common Base

   Depending which terminal is common between both input and output or at ground potential.



**Common Emitter, Common Collector, Common Base**

# Common Emitter Configuration

 


Three regions:


- Active(linear) region
- Saturation region
- Cutoff region

Linear region → Amplification

Saturation and cut-off → Switching

 

Output characteristics

 

Input characteristics

# Limits of Operations

The maximum power dissipation in a transistor is given by:

$$P_{cmax} = V_{CE} \times I_C$$

e.g if  $V_{CE}$  is 10V and  $I_C = 30\text{mA}$ , then  $P_{cmax} = 300\text{mW}$ .

- Ensure that the maximum ratings are not being exceeded.
- Output signal should be with minimum distortion.
- Refer to current – voltage characteristics and data sheet before designing the circuits.

Example from data sheet

$$I_{Cmax} = 50\text{mA}$$


$$V_{CE0} = 20\text{V}$$

$$P_{cmax} = 300\text{mW}$$


$$V_{CEsat} = 0.3\text{V}$$

$$I_{CEO} = 10\mu\text{A (base open)}$$

 $I_{CEO} = \beta I_{CBO}$  (emitter open) mainly leakage current for common emitter configuration



Maximum current

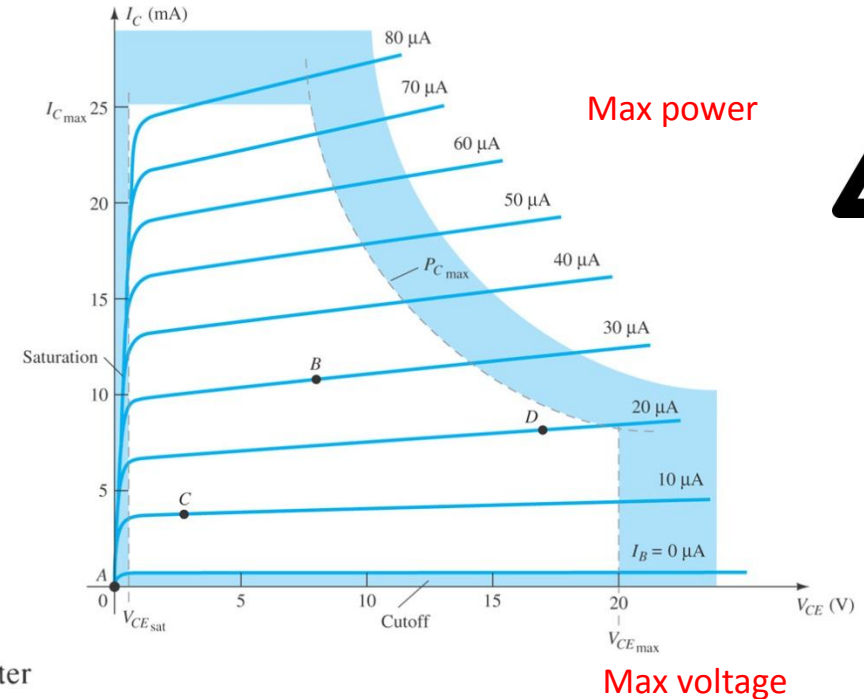

$$I_{CEO} \leq I_C \leq I_{Cmax}$$

$$V_{CEsat} \leq V_{CE} \leq V_{CEmax}$$

$$I_C \times V_{CE} \leq P_{cmax}$$

# Transistor Biasing

## Chapter 4

- Biasing is applying DC supply to power the circuit.
- The desired operating point is established by the DC bias network.
- Biasing network will also determine the stability of the circuit against variations in temperature or changes in the value of  $\beta$

$\beta$  = common emitter forward current amplification factor

$$\beta_{dc} = \frac{I_C}{I_B} = \frac{mA}{\mu A} \quad (\text{typical value between 100 to 300})$$

$$\beta_{ac} = \frac{\Delta I_c}{\Delta I_b} \quad (\text{output current / input current})$$

$$I_E = I_C + I_B = \beta I_B + I_B = I_B(1 + \beta)$$

The value of  $\beta$  is given by the transistor data sheet  
Or can be calculated from the IV curves.

# Load line and operating point

The network equation is defined by the DC biasing circuit. To draw the load line that represent the network equation on the output characteristics of the BJT transistor, the collector emitter loop equation is:

$$V_{CC} = I_C R_C + V_{CE} \quad (\text{Kirchhoff's Voltage Law , KVL*})$$

Now assume  $I_C = 0 \text{ mA}$  , then  $V_{CE} = V_{CC}$  this represent the first point on the curve

For  $V_{CE} = 0$ ,  $I_C = V_{CC}/R_C$  this represent the second point on the curve

By joining the two points, the load line is constructed, and the intersection with  $(I_C - V_{CE})$  transistor characterises showing all possible operating points.



The operating point Q can be fixed by the values of  $R_C$  and  $R_B$ :

$$R_C = \frac{V_{CC} - V_{CEQ}}{I_{CQ}}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_{BQ}}$$

$I_{CQ}$  and  $V_{CEQ}$  are the collector current and collector-emitter voltage at the operating point Q,

  $I_{BQ}$  is the base current at the operating point Q





Output characteristics


*\*KVL law is based on the conservation of energy whereby voltage is defined as the energy per unit charge. The total amount of energy gained per unit charge must be equal to the amount of energy lost per unit charge, as energy and charge are both conserved.*
  
# Load line adjustment


The operating point Q can be adjusted by changing  $R_C$ ,  $R_B$  or  $V_{CC}$




$$R_B = \frac{V_{CC} - V_{BE}}{I_{BQ}}$$

 
 
$$R_C = \frac{V_{CC} - V_{CEQ}}{I_{CQ}}$$




# DC biasing circuits

 


(a)

Fixed bias

 


(b)

Emitter bias

 

(c)

Feedback  
bias

 

(d)

Voltage  
divider bias

# Fixed Bias Configuration

Base –Emitter loop (KVL)

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$R_B$  sets the level of base current for the operating point


Collector- Emitter loop (KVL)

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$R_C$  value determine the level of  $I_C$

$$V_{CE} = V_{CC} - I_C R_C$$

 



# Improved Bias stability

To improve the stability of the transistor circuit against variations in the value of  $\beta$  and temperature, a resistor is inserted between the emitter terminal and ground called  $R_E$ .

## Base-Emitter Loop:

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\text{Substitute for } I_E = (\beta + 1) I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\text{Then solve for } I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$


## Collector-Emitter Loop:

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$


$$\text{But } I_E \approx I_C$$

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0$$
 
$$\text{Solve for } I_C = \frac{V_{CC} - V_{CE}}{(R_C + R_E)}$$



Input loop

 

Output loop

# Voltages across the transistor device

$$V_E = I_E R_E \approx I_C R_E$$

$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$


OR

$$V_C = V_{CC} - I_C R_C$$

$$V_{BE} = V_B - V_E$$

$$V_B = V_{BE} + V_E$$

$$V_B = V_{CC} - I_B R_B$$

 

$V_{BE} = 0.7V$  for Silicon Transistor, given by data sheets. For different semiconductors,  $V_{BE}$  is different and highly dependent on the Energy gap of the material

# Feedback Bias

## Base –Emitter Loop:

$$V_{CC} - I_C' R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_C = \beta I_B$$

$$I_C' = I_C + I_B = I_E$$

$$\text{But } I_C \gg I_B$$

$$I_C' \approx I_C \approx I_E = \beta I_B$$

**Then:**

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$


$$\text{Solve for } I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

The feedback path results in a reflection of the resistance  $R_C$  back to the input loop

Now if  $\beta(R_C + R_E) \gg R_B$

$$I_B \approx \frac{V_{CC} - V_{BE}}{\beta(R_C + R_E)}$$
 
$$I_C = I_B \beta = \frac{V_{CC} - V_{BE}}{(R_C + R_E)} \quad \text{i.e } I_C \text{ is independent on } \beta \text{ when } \beta(R_C + R_E) \gg R_B$$



# Feedback Circuit output loop

Collector-Emitter loop:

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$


$$\text{Since } I_C = I_E \approx I_C, I_C \gg I_B$$

$$V_{CC} = I_C R_C + V_{CE} + I_C R_E$$


$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

And

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$


 


# DC biasing

 


$$I_B, I_C, I_E, V_{CE}$$

Thevenin

  


$$\therefore I_E = I_B (\beta + 1)$$

 

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$
 
$$\text{Solve for } I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$



$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$I_C \simeq I_E$$

$$I_C = \frac{V_{CC} - V_{CE}}{(R_C + R_E)}$$


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = V_C - V_E$$

$$V_E = I_E R_E$$

$$V_{BE} = V_B - V_E$$

# Transistor switching


 


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$(1) I_B = \frac{V_i - V_{BE}}{R_B}$$

for  $V_i = 0$ ,  $I_B = 0$ ,  $I_C = 0$   
 $V_{out} = V_{CC} = \text{High level}$

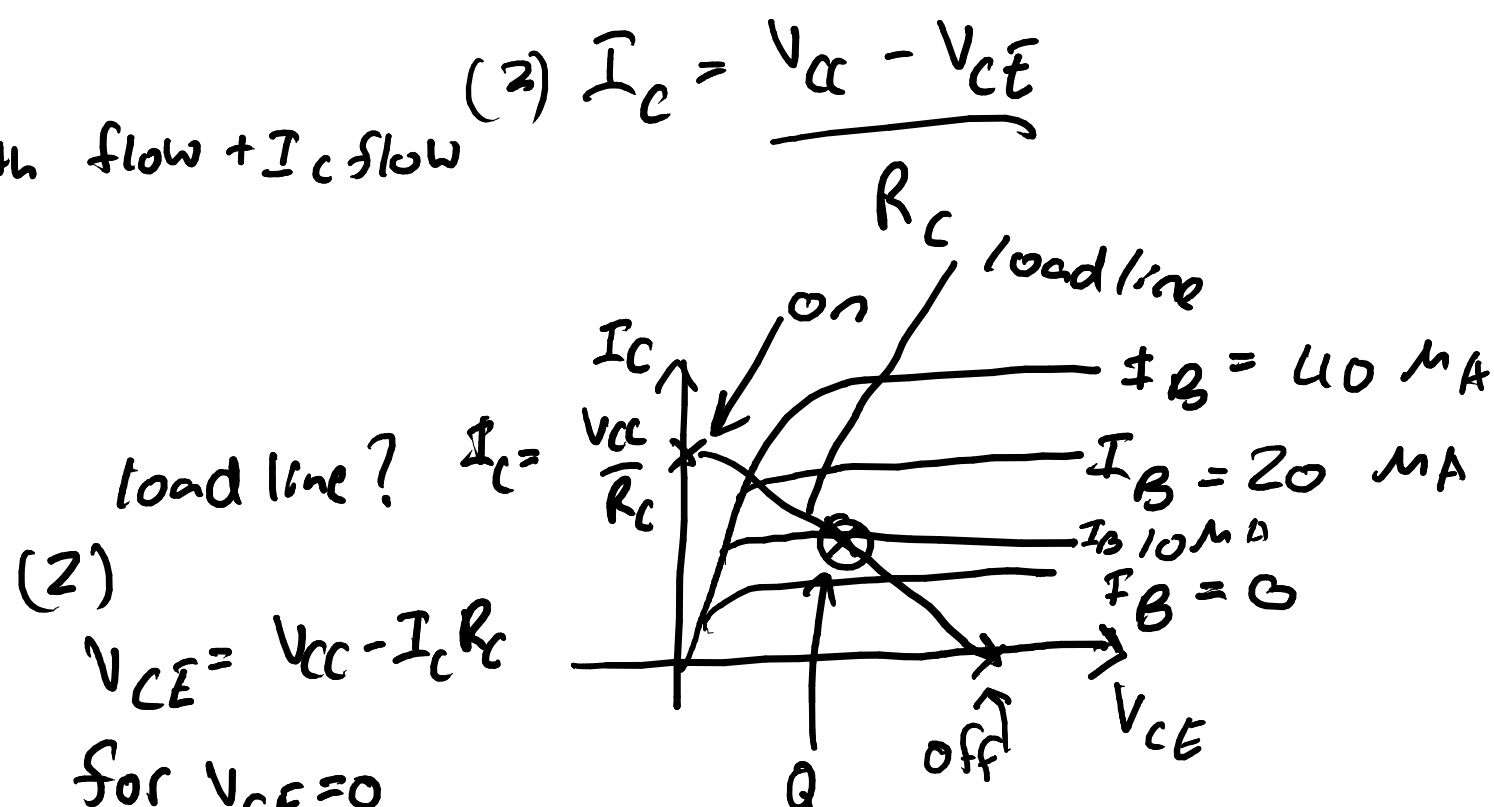 for  $V_i = \text{High (logic) level}$ ,  $I_B$  with flow +  $I_C$  flow  
 $V_o = 0V$ , low level



(2)  $V_{CE} = V_{CC} - I_C R_C$   
 for  $V_{CE} = 0$   
 $I_C = \frac{V_{CC}}{R_C}$   
 for  $I_C = 0$   
 $V_{CE} = V_{CC}$

Switch  
 either 'on' or 'off'

To ensure transistor is on


(1)  $I_C = \frac{V_{CC}}{R_C} = I_{C \text{ sat}} = ?$

(2)  $I_C = \beta I_B$

(3)  $I_B = \frac{V_i - V_{BE}}{R_B}$  calculate  $I_B$  (3)  
 $V_{BE} = 0.7V$
 
# Voltage Divider Bias



A bias circuit that is less sensitive to variations in the value of  $\beta$  by essentially reducing the effective value of  $R_B$



$$R_B = R_1 // R_2$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

  
Using Thevenin's equivalent circuit for the left hand side of the circuit shown:




Equivalent circuit




# Applying Thevenin's Equivalent Circuit

 

 Using Voltage Divider rule to find  $V_{R_2} = E_{Th}$



 Find the equivalent resistance  $R_{Th}$  of the circuit with  $V_{CC} = 0$



Redraw the circuit with  $E_{Th}$  and  $R_{Th}$  and calculate  $I_B$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (1 + \beta)R_E} \dots\dots(3)$$

Applying Kirchhoff's voltage law;

$$E_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0$$

$$I_E = (1 + \beta) I_B$$

$$E_{Th} - I_B R_{Th} - V_{BE} - (1 + \beta) I_B R_E = 0$$

Then solve for  $I_B$  equation(3)

# Output Loop

**Collector-Emitter loop:**

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

Since  $I_C \approx I_E$ ,  $I_C \gg I_B$

$$V_{CC} = I_C R_C + V_{CE} + I_C R_E$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

**Voltages across the transistor:**

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = V_C - V_E$$


$$V_E = I_E R_E$$

$$V_{BE} = V_B - V_E$$

$$V_B = V_{BE} + V_E$$

$$V_C = V_{CC} - I_C R_C$$

$V_{BE} = 0.7V$  for Si transistors

 

# Transistor Switching



To ensure the transistor is switched ON

$$I_C = \beta I_B \geq I_{C\text{sat}}$$



$$I_{C\text{sat}} = V_{CC} / R_C \quad \text{highest collector current}$$

$$V_{CE} = V_{CC} - I_C R_C \quad \text{from the output loop}$$
  
$$I_B = (V_i - V_{BE}) / R_B \quad \text{from circuit input loop}$$



Input voltage

  

Output voltage

# Transistor Switching

Consider applying a square waveforms at the base terminal of the BJT circuit shown:

(1) At  $V_i = 0V$  (low voltage level)

$$I_B = \frac{V_i - V_{BE}}{R_B} = 0 \text{ as there is no current flowing for input voltage} = 0V.$$

As  $V_{BE} = 0V$ ,  $I_B = 0$ ,  $I_C = 0$ , **Transistor is OFF**


$V_{CE} = V_{out} = V_{CC} = 10V$  ( no current is flowing in the collector therefore output voltage is high)

(2) At  $V_i = 10V$  (high voltage level) ,  $V_{BE}$  will be 0.7V

$$I_B = \frac{V_i - V_{BE}}{R_B} \text{ will be flowing and } I_B \text{ value is determined by } R_B$$

Then  $I_C$  will be flowing and has high value, the **Transistor is switched ON**, output voltage is small as the output is exposed to ground

 $V_{CE} = V_{out} \sim 0V$  , low voltage state,  
( practically  $V_{CEsat} = 0.15 - 0.2V$ )



# To ensure transistor is ON in Saturation


$$\text{Calculate } I_B = \frac{V_i - V_{BE}}{R_B} \dots\dots\dots(1)$$

$$\text{Then calculate } I_B = \frac{I_{C \text{ sat}}}{\beta} \dots\dots\dots(2)$$

$$I_{C \text{ sat}} = \frac{V_{CC}}{R_C} \dots\dots\dots(3)$$

To ensure that the transistor will be working in saturation region (ON state)

 The base current  $I_B$  calculated from equation 1 must be larger than  $I_B$  calculated from equation 2. This is usually determined by the value of the resistance used in the base terminal  $R_B$ .



# Example

If  $R_C = 0.82k\Omega$  and  $R_B = 63k\Omega$

Is the transistor in saturation or cut off mode for the input voltage shown:

$$I_{csat} = V_{CC}/R_C \quad \text{as } V_{CE} \text{ is very small in saturation region } V_{CC} = I_{csat} R_C + V_{CEsat}$$

For saturation condition to establish, the level of  $I_B$  must be made:

$$I_{Bmin} \geq \frac{I_{csat}}{\beta_{dc}} \quad \text{to ensure saturation}$$



$$\text{Now for } V_i = 5V, \quad I_B = \frac{V_i - V_{BE}}{R_B} = \frac{5 - 0.7}{63k} = 68 \mu A \text{ from the circuit}$$

$$I_{csat} = \frac{V_{CC}}{R_C} = \frac{5V}{0.82k} = 6.1mA$$

$$I_B = 68 \mu A > \frac{I_{csat}}{\beta_{dc}} = \frac{6.1mA}{100} = 61 \mu A$$

Using transistor with higher  $\beta$  will ensure saturation

  $68 \mu A > 61 \mu A$  then the transistor is in saturation



$$R_{sat} = \frac{V_{CEsat}}{I_{csat}} = \frac{0.15V}{6.1mA} = 24.6 \Omega \quad (\text{transistor has low resistance when ON})$$

Now if  $V_i = 0V$ , Transistor is OFF,  $I_B = I_C = 0mA$

$$R_{cutoff} = \frac{V_{CC}}{I_{CEO}} = \frac{5V}{10\mu A} = 500k\Omega \text{ very high resistance in cut-off region.}$$

$I_{CEO}$  is the minority carriers current flowing in the reverse bias collector emitter junction.