
 


Enhancement MOSFET structure

 

SS, Body
To reference all devices on the Si chip to same voltage level for triggering


Induced channel $V_{GS} > V_T$
Negative charge electrons attracted by the positive gate voltage from an n type like channel allowing I_D to flow



Bio Transistor based on FET technology

Switching Applications of MOS and CMOS Devices



- MOS devices are characterised by their low power consumption
- High Input Impedance
- Ability to form Transistors, Diodes, Capacitors and Resistors from their structure, hence, integrated circuits are constructed from transistors only structure.
- Easy to manufacture, simple device structure, can relate device performance (I_D and g_m) to device materials and dimensions.
- Easy to integrate to ultra high scale (ULSI), 7.2 billion transistors per chip(2016).
- Scaling down to nanometre scale is possible, currently (2019) 7 nm technology is available by AMD, TSMC and Samsung
- Can be made from Silicon

 

Transistor evolution

MOORE'S LAW

 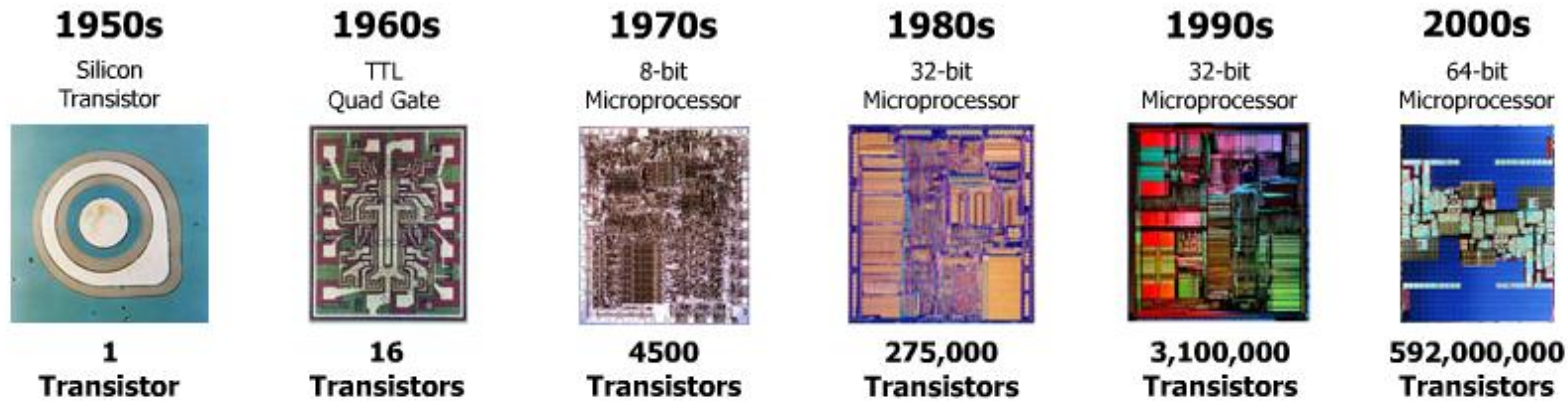"Transistor density on integrated circuits doubles about every two years." *




7.2 billion transistors, 2016

* Source : Samsung Electronics Co., Ltd.

*V_{dd} : Supplying voltage of drain

Transistors gate length

 



More functionality, continuous development

Evolution of the Mobile Phone




FinFET

Fully Depleted Tri-Gate Transistor

  


FinFET structure cross section and side view

Tri-Gate Transistor
Fully Depleted

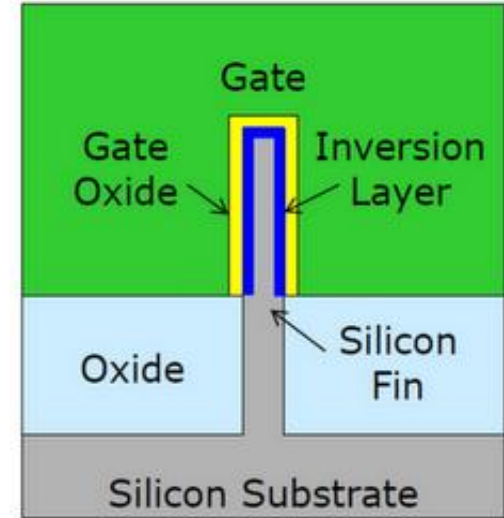


Transistor Gate Delay

 

22 nm 3-D Tri-Gate transistors provide improved performance at high voltage and an *unprecedented* performance gain at low voltage

Speed and threshold voltage of FinFET

Transistor Fin Improvement

 




22 nm 1st Generation
Tri-gate Transistor




14 nm 2nd Generation
Tri-gate Transistor

SEM image of FinFET developed by Intel

D Mosfet - pull up resistor

   


- Drain is V_o
- Gate is V_i

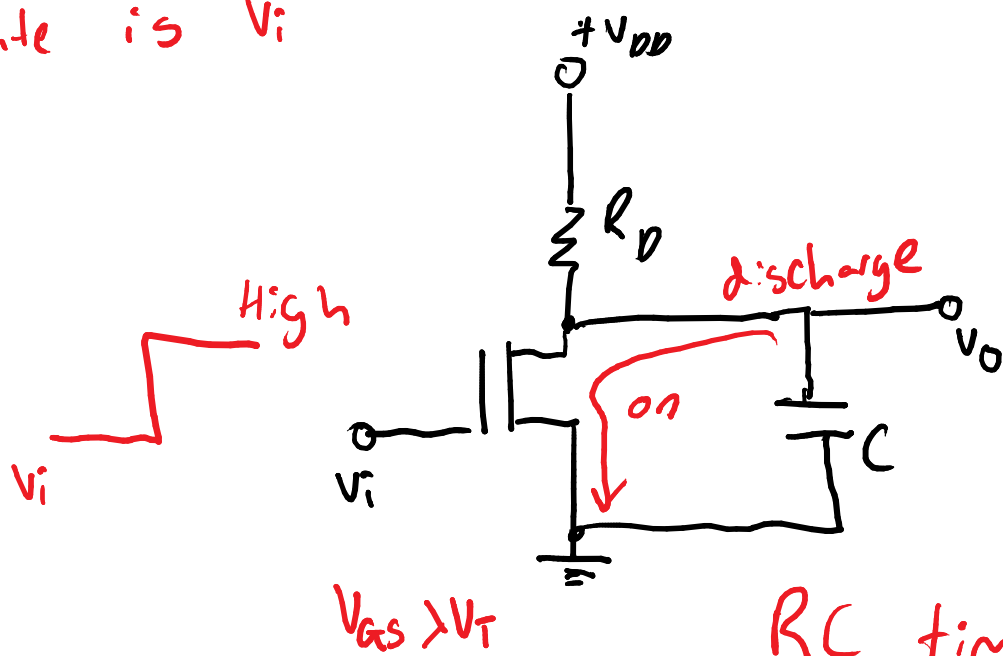

RC time constant will determine the switch speed


R_{on} of the transistor is 1Ω

 


Capacitor charging through R_D .

Time constant $R_D \cdot C$
pull up resistor

Basic MOSFET Inverter


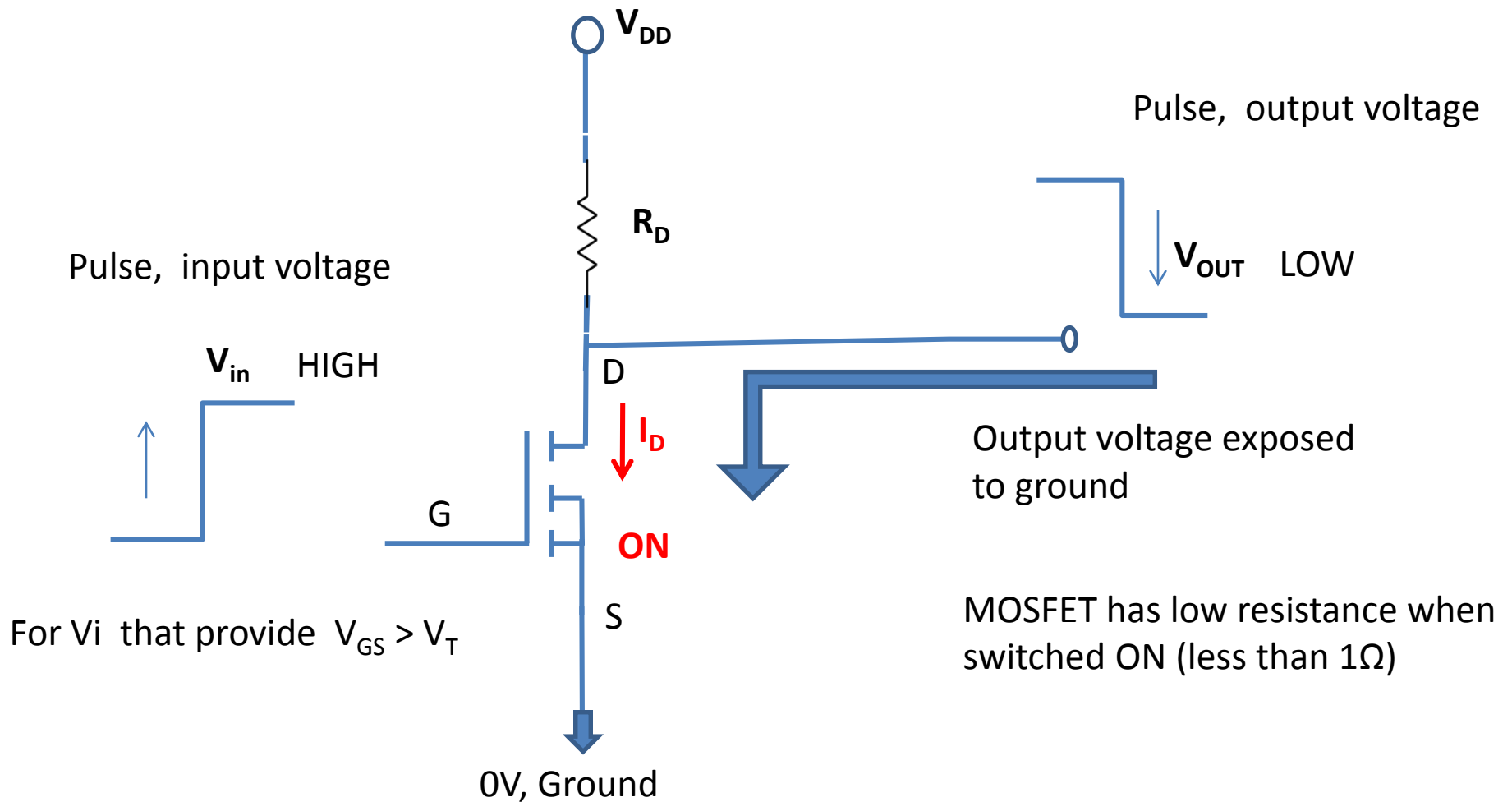


Basic MOSFET Inverter

 

MOSFET INVERETER Switching time

  
- For LOW input the output is HIGH
- For HIGH input the output is LOW
- This is a typical inverter action



Symbol for Inverter

Output V_{OUT} is inverted relative to the input pulse V_{IN}



Time delay

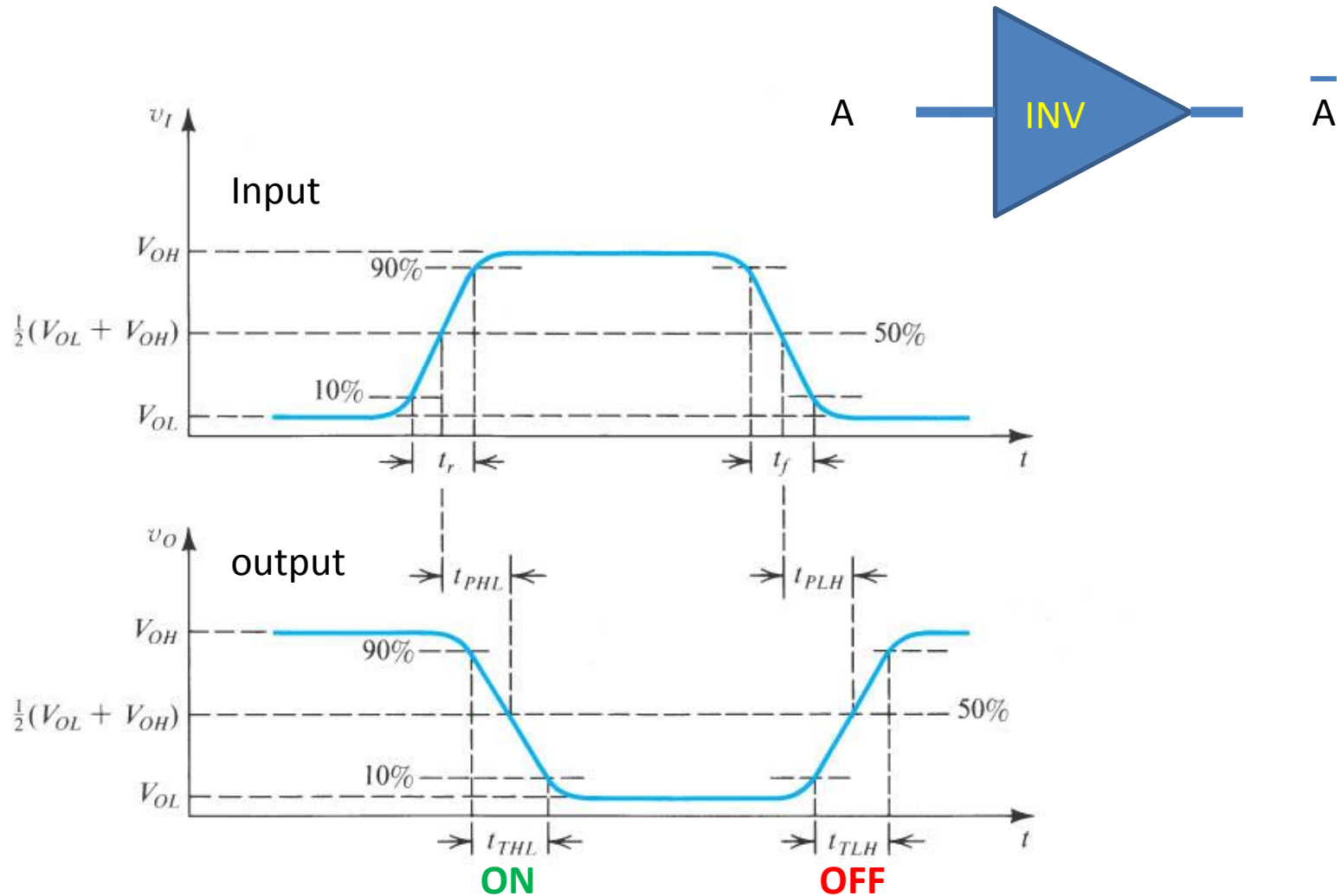

Delay times associated with ON and OFF switching


t_r is the rise time, t_f is the fall time, time it takes to go from 10% to 90% of pulse height
 t_{THL} and t_{TLH} are the time for the pulse to go from high to low and from low to high respectively.

  Voltage Transfer Curve VTC for MOS Inverter




V_{OH} High Level output voltage
 V_{OL} Low Level output voltage
 V_{IL} Low Level input voltage
 V_{IH} High Level input voltage

MOSFET Inverter with capacitive load C_L

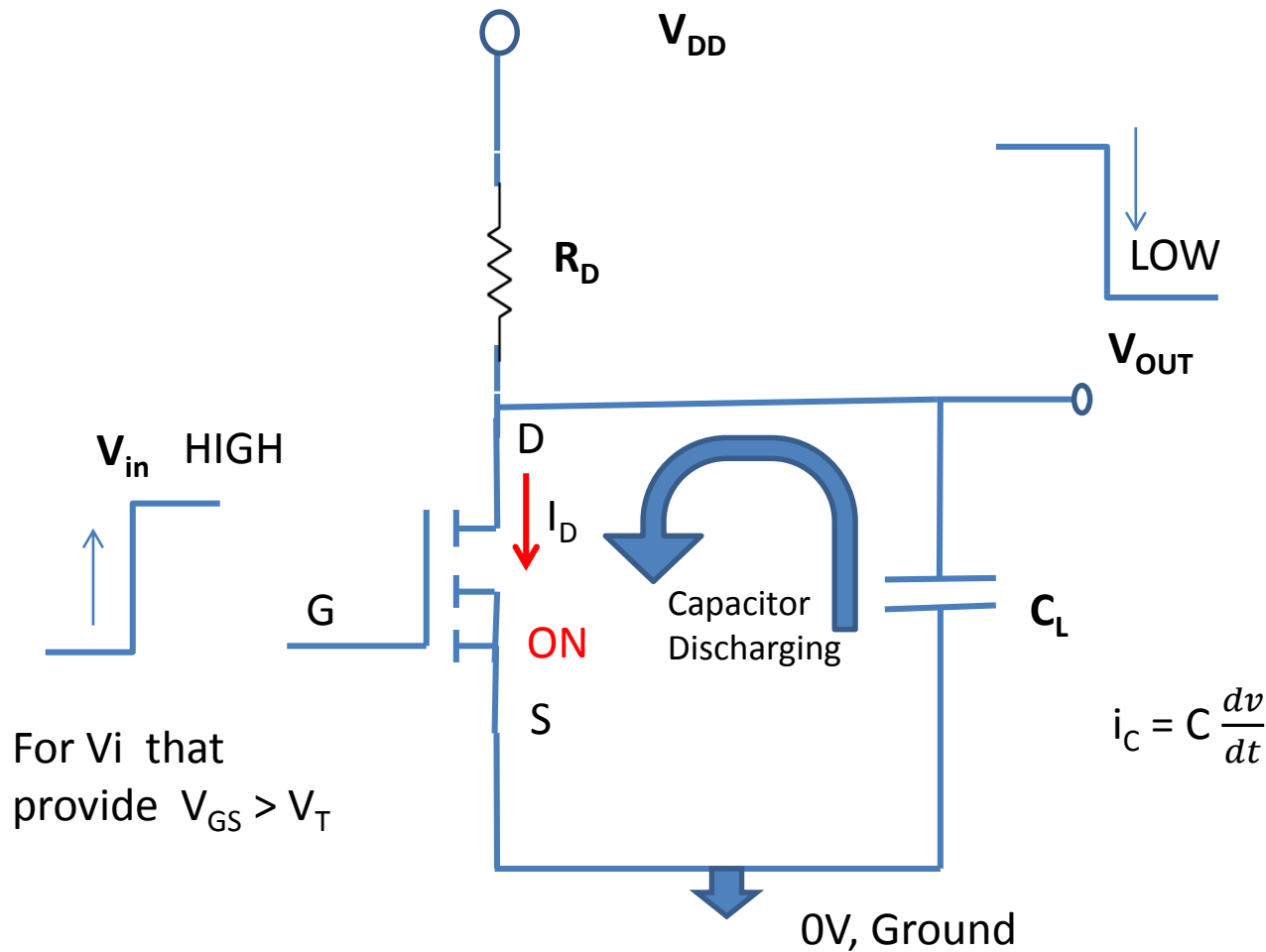


Capacitor is discharging to ground through the ON switched FET, time constant = $R_{on} \times C_L$
Switching speed is determined by how fast the capacitive load charge and discharge

V_{in} LOW , capacitor charging

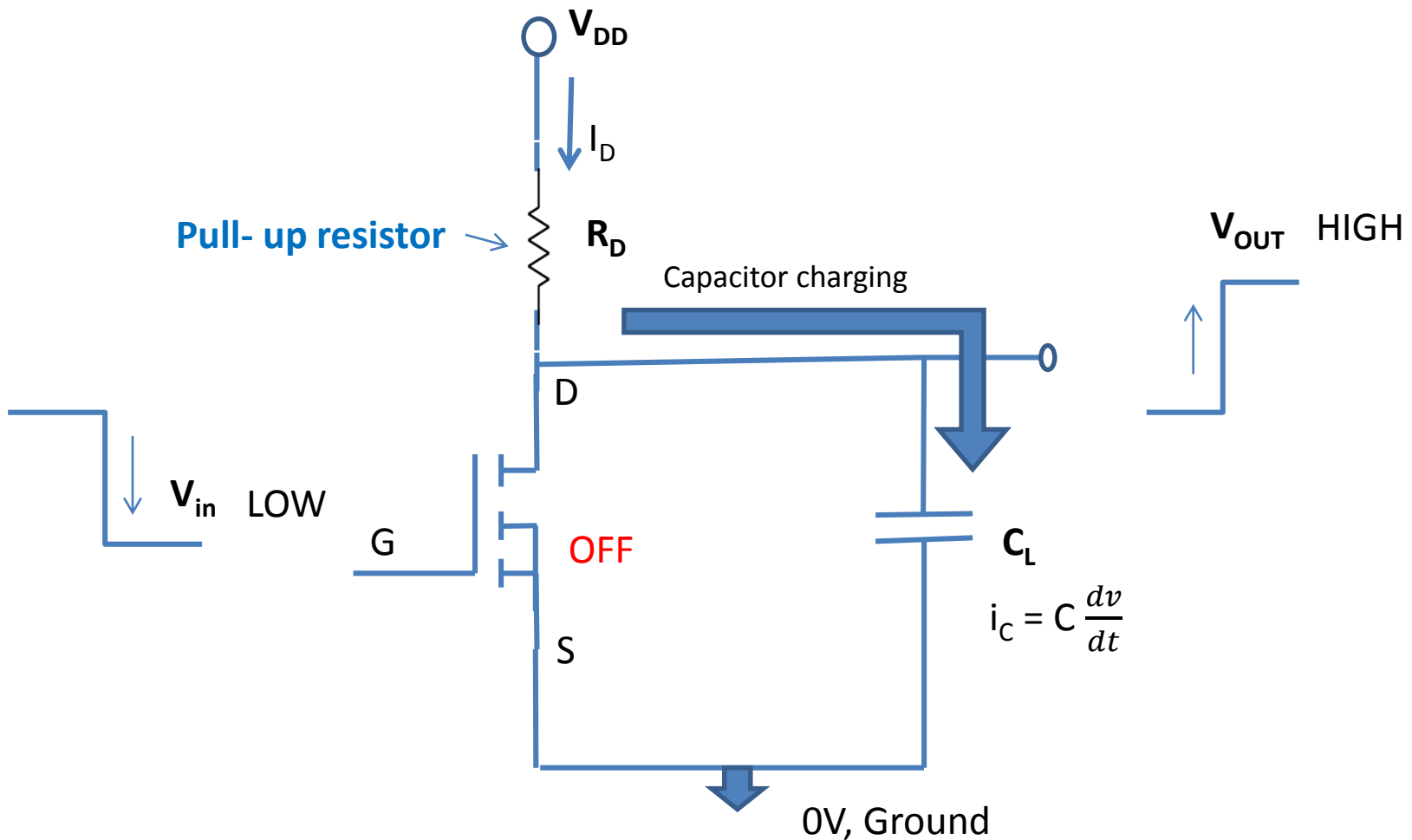

Capacitor is charging through the pull-up resistor R_D to V_{DD} , Time constant = $C_L \times R_D$

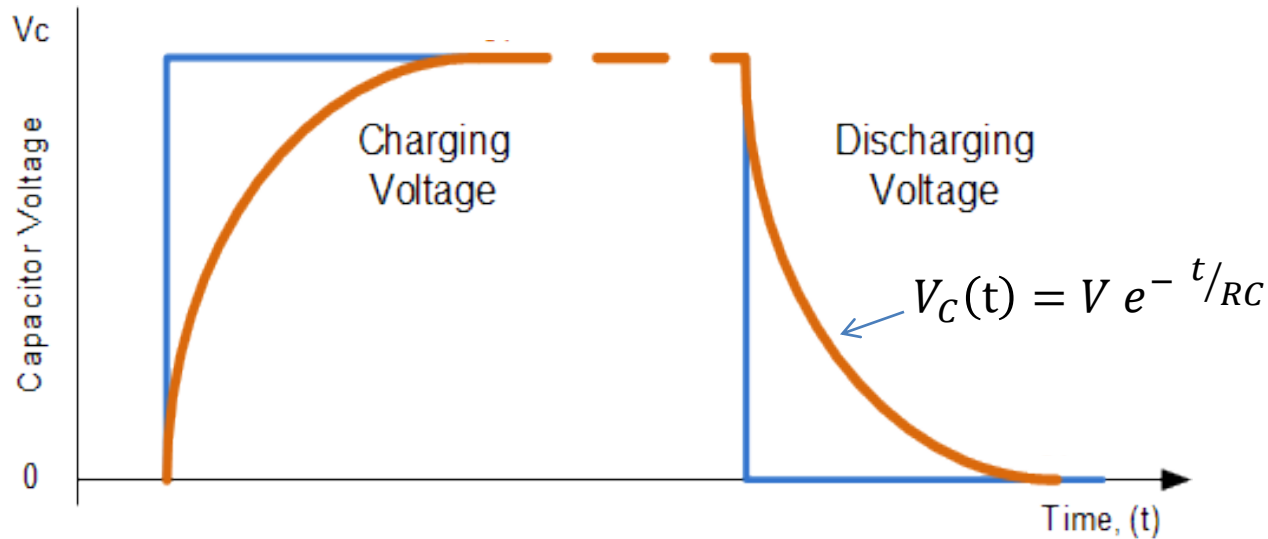Capacitor charging and discharging waveforms




Charging and discharging time depending on the $R \cdot C_L$ time constant

$$C = \frac{\epsilon_o \epsilon_r}{t_{ox}} A$$

Value of capacitor is determined by the area of device and dielectric properties of the material.


R is determined by the ON resistance of the MOSFET(On state) or the pull up resistor(Off state)

NMOS Switch and DMOS load

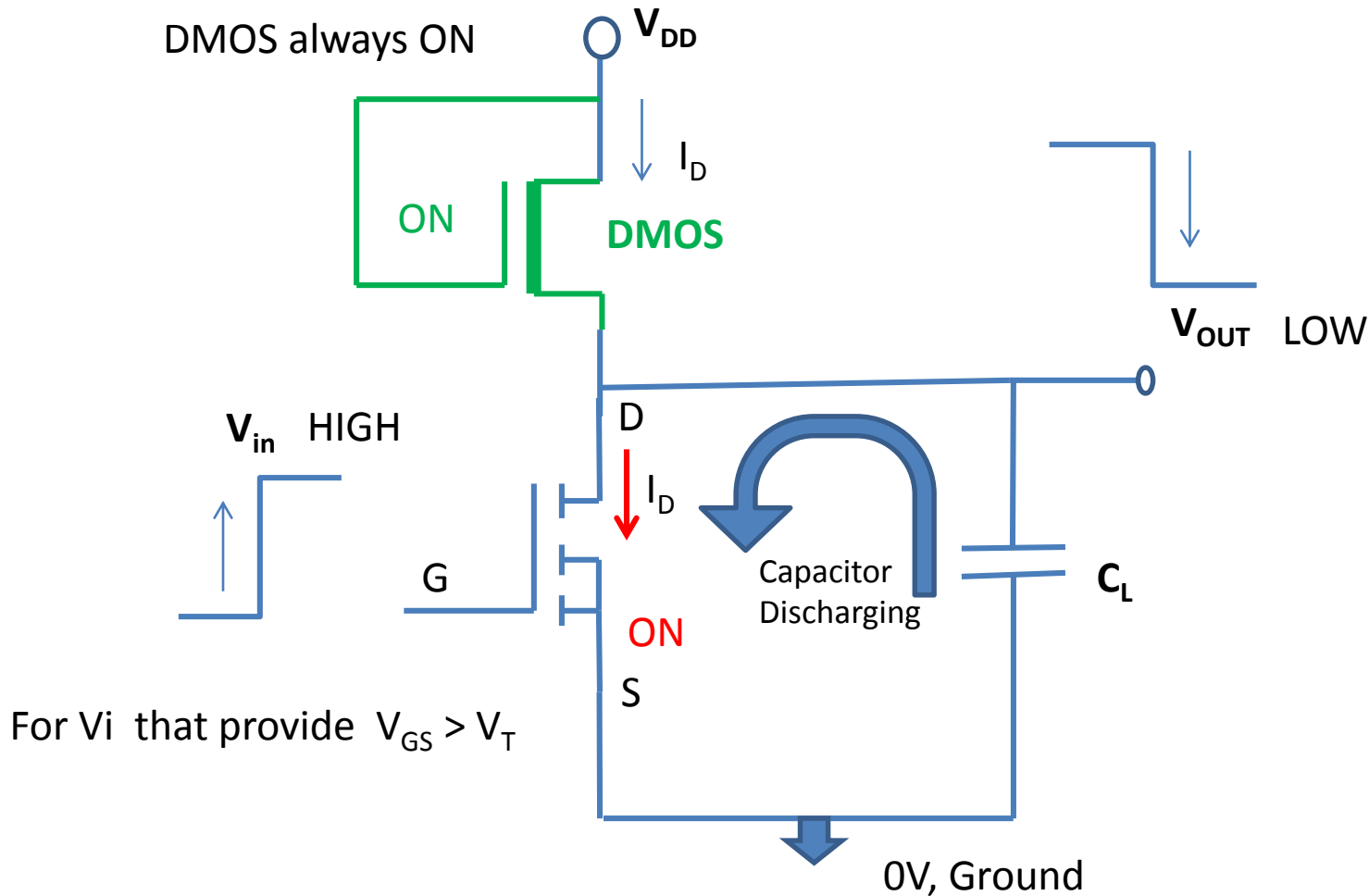

DMOS is used as a pull-up resistor, EMOS as switch


EMOS – DMOS Inverter

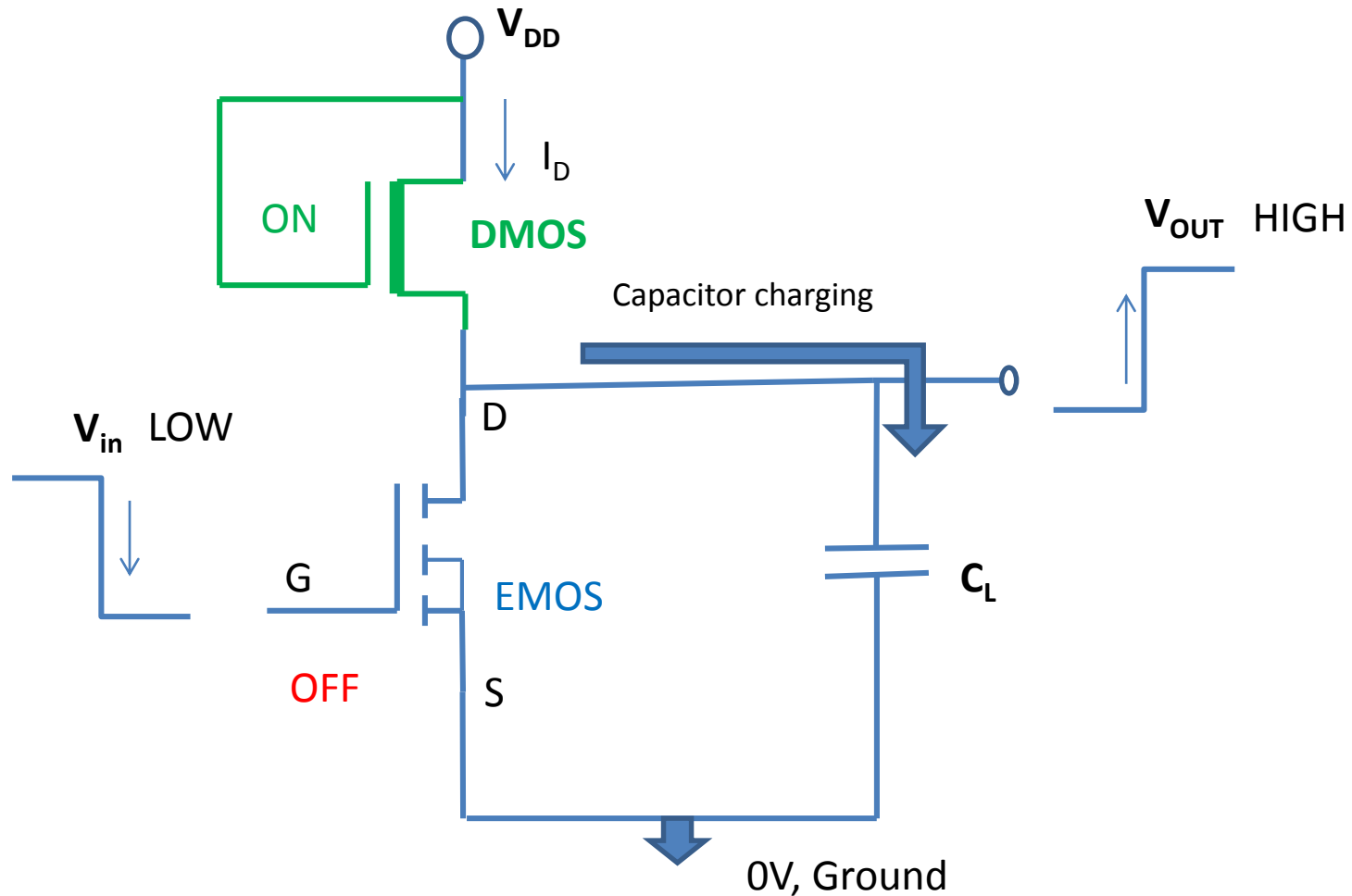

When the EMOS is OFF, the capacitor is charging through the DMOS to V_{DD}


Inverter circuits

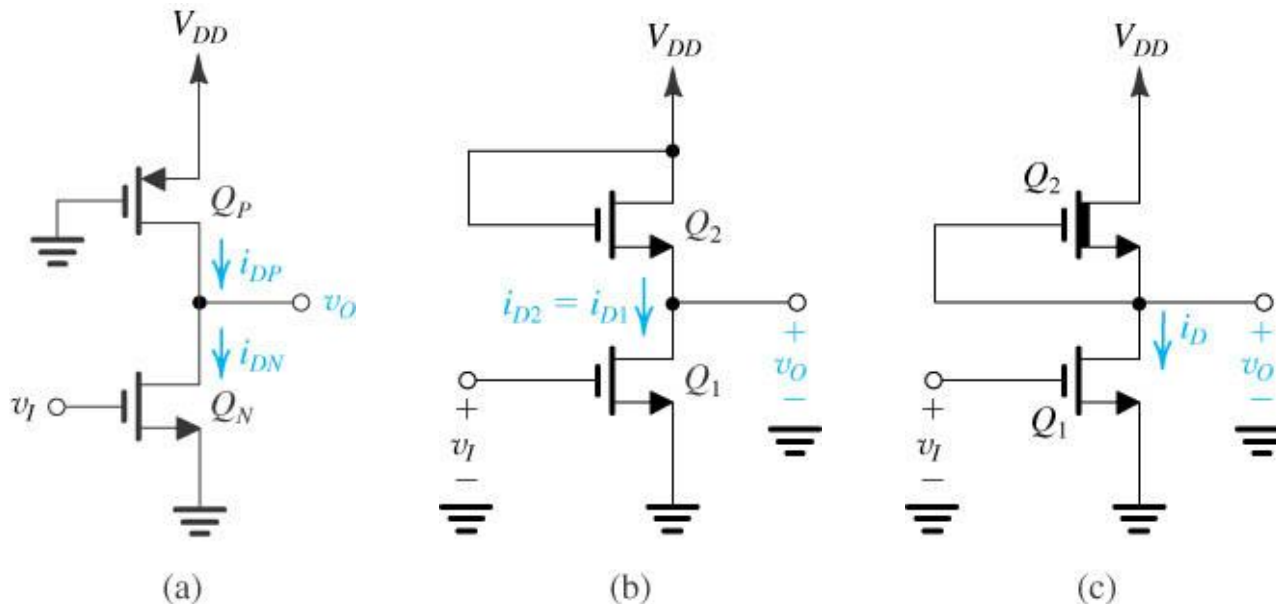Inverters constructed with three design approaches



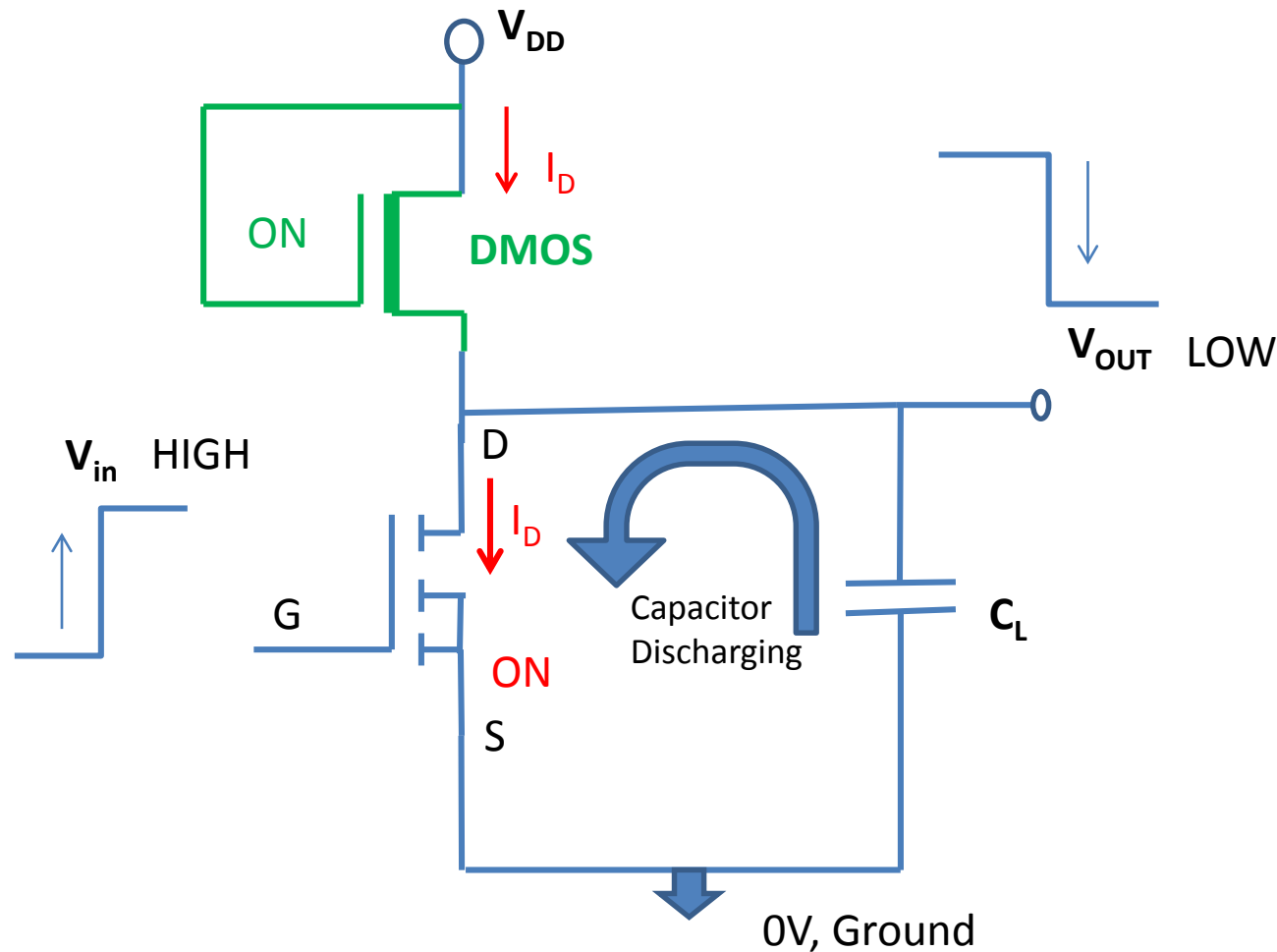- a) Inverter with PMOS and NMOS configuration
- b) Inverter with two NMOS FETs, Q_2 is acting as the pull-up resistor
- c) Inverter constructed with EMOS(Switch) and DMOS resistive, pull up transistor


Power consumption problem with DMOS, EMOS inverters



When the EMOS is ON, the DMOS is also ON, exposing the power supply to ground and the power consumption is high .

Basic CMOS Inverter

 
Complementary Metal Oxide Semiconductor Technology
Uses EMOS in both PMOS (resistive load) and
NMOS(switch)configurations .



When the input voltage is HIGH and larger than the threshold voltage V_T
The NMOS is switched ON, V_{OUT} is LOW,
The PMOS is OFF, cutting V_{DD} from ground
reducing power consumption.


CMOS inverter

 Complementary Metal Oxide Semiconductor (CMOS) FET




When the input voltage V_{IN} is LOW
NMOS is **OFF**
PMOS is **ON** and pulling the output voltage
 V_{OUT} to V_{DD} (HIGH).

CMOS Loading

 

 
Capacitive load, charging through the PMOS, Discharging through the NMOS, the ON resistances of the PMOS and NMOS will determine the switching speed



CMOS driver, CMOS load


Output of driver is input to the load. Input is through the gate which is isolated from the channel with oxide, ie capacitive load.

Basic Digital Gates

 


NOR gate

$$Y = \overline{A+B}$$

 


NAND gate

$$Y = \overline{A.B}$$

 


Implementation of
a Boolean function

$$Y = \overline{A + B.C}$$

 

$$V_{OUT} = \overline{V_{IN}}$$


CMOS Non-Inverting case

 


Output follow the input, No inversion

4 input NOR gate implemented using CMOS technology

 The output (y) is LOW when either inputs (A OR B OR C OR D) are high




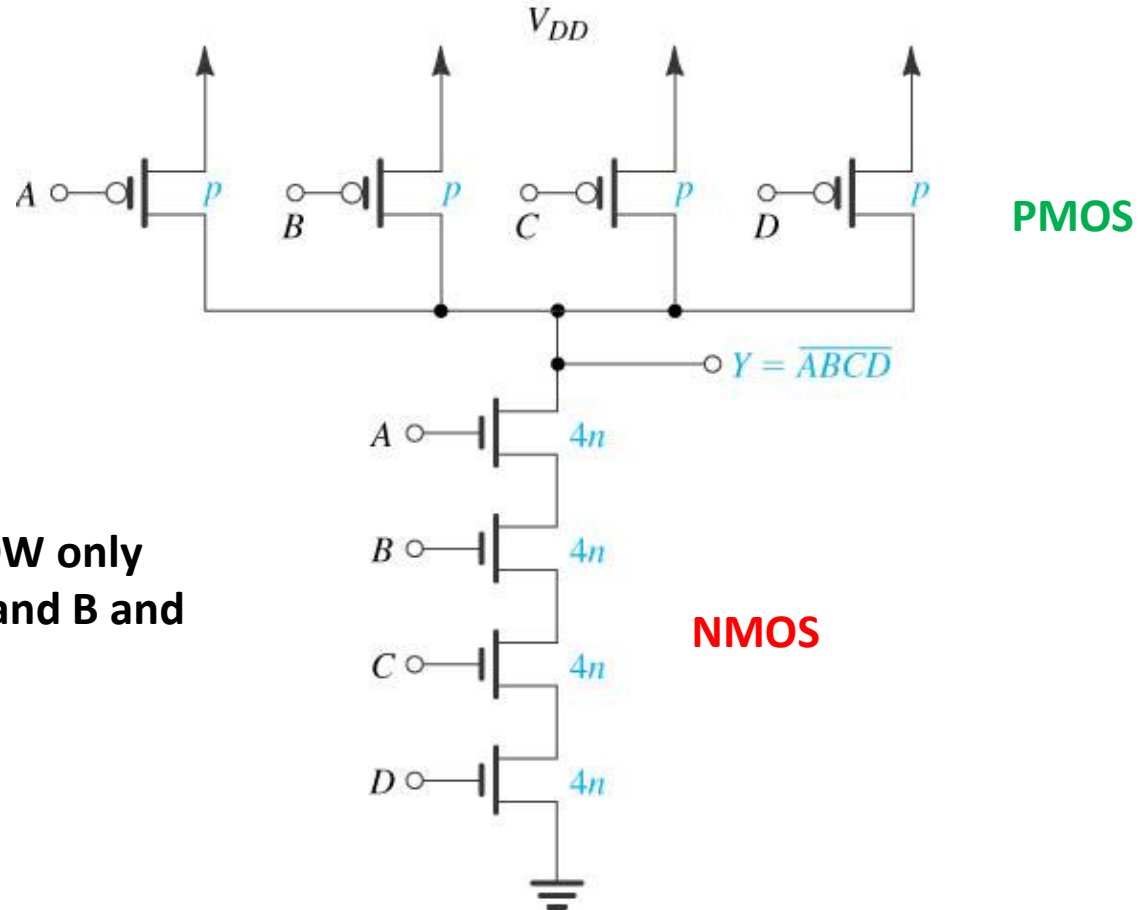
4 input NAND gate implemented using CMOS technology



The output (y) is LOW only when all inputs (A, and B and C and D) are High

CMOS NAND and NOR gates

CMOS NAND gate

 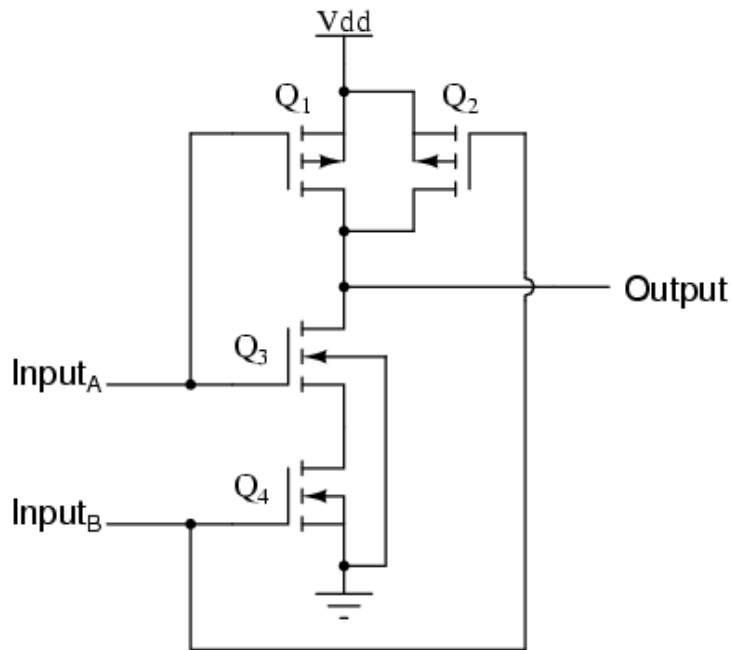

CMOS NOR gate

